

Total No. of Questions : 8]

SEAT No. :

P1486

[Total No. of Pages : 2

[6002]-113

S.E. (Electronics/Electronics & Computer/E & TC)

DIGITAL CIRCUITS

(2019 Pattern) (Semester - III) (204182)

Time : 2½Hours]

[Max. Marks : 70

Instructions to the candidates:


- 1) Answer Q.No.1 or Q.No.2, Q.No.3 or Q.No.4, Q.No.5 or Q.No.6, Q.No.7 or Q.No.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicates full marks.

- Q1)** a) Explain the working of a half-adder? Draw its logic diagram. [7]
b) Implement the full subtractor using a 1 : 8 demultiplexer. [5]
c) Implement the following function using multiplexer
 $f(A,B,C) = \sum m(0, 2, 4, 6)$. [5]

OR

- Q2)** a) Draw the logic diagram of full-adder and its truth table. [7]
b) Implement a full-adder using Demultiplexer. [5]
c) Implement the given logic function using a 4 : 1 multiplexer.
 $f(A,B,C) = \sum m(0, 2, 4, 6)$. [5]

 - Q3)** a) For the state diagram shown in figure, obtain the state table and design the circuit using minimum number of J = K flip - flops. [8]




- b) Explain the function of a shift register. Give its application. [5]
c) Explain with truth table the working of clocked RS flip-flop. [5]

OR

- Q4)** a) Design a sequence generator using T FFs $0 \rightarrow 1 \rightarrow 7 \rightarrow 4 \rightarrow 2$. [8]
b) Explain the types of shift register. [5]
c) Explain with diagram the working of D type Flip-flop. Give its truth table. [5]

P.T.O.

 - Q5) a)** Design the clocked sequential circuit for the state diagram using JK flip flop. [9]



- b) Draw ASM chart for a 2 bit up-down counter having mode control input M.
M=1 Up counter.
M = 0 Down Counter. [8]

OR

- Q6) a)** Design a sequential circuit using Mealy machine for detecting the sequence.....1001.....Use Jk Flip-flop. [9]
- b) Explain in short: [8]
- State Diagram.
 - ASM chart.

- Q7) a)** Explain the classification of memories based on their principle of operation. [8]
- b) Write a short note on concept of PLA and PAL. [10]

OR

- Q8) a)** Explain with circuit diagram the dynamic MOS memory. [8]
- b) A combinational circuit defined by the function. [10]
- $$F_1(A, B, C) = \sum (3, 5, 6, 7) \text{ and } F_2(A, B, C) = \sum (0, 2, 4, 7)$$
- Implement the circuit with PLA having 3 inputs, 3 products terms and 2 out puts.

★ ★ ★